

Electrical Network Analysis (EE-241)


Assignment # 6, Spring 2021

Submission Deadline: **Thursday** July 15, 2021

Maximum Marks: 100


- Submit at the start of the class on Thursday (15th July 2021).
- Write down your roll number on each page at the top right corner and staple properly.
- Use pencils to draw the circuit diagrams.

- Let $h(t) = 2e^{-3t}u(t)$ and $x(t) = u(t) - \delta(t)$. Find $y(t) = h(t) \star x(t)$ by
 - using convolution in the time domain
 - finding $H(s)$ and $X(s)$ and then obtaining inverse Laplace Transform of $H(s)X(s)$
 - If a network is found to have the transfer function $H(s) = \frac{s}{s^2+8s+7}$, determine the s-domain output voltage for $v_{in}(t)$ equal to
 - $3u(t)$ V
 - $25e^{-2t}u(t)$ V
 - $4u(t+1)$ V
 - $2 \sin 5t$ V
 - A particular network is known to be characterized by the transfer function $H(s) = \frac{s+1}{s^2+23s+60}$. Determine the critical frequencies of the output if the input is
 - $2u(t) + 4\delta(t)$
 - $-5e^{-t}u(t)$
 - $4te^{-2t}u(t)$
 - $5\sqrt{2}e^{-10t}\cos 5t u(t)$
- For each of the two networks shown in Figure 1, write the **Transfer Functions** $H(s)$ and determine their **poles** and **zeros**.

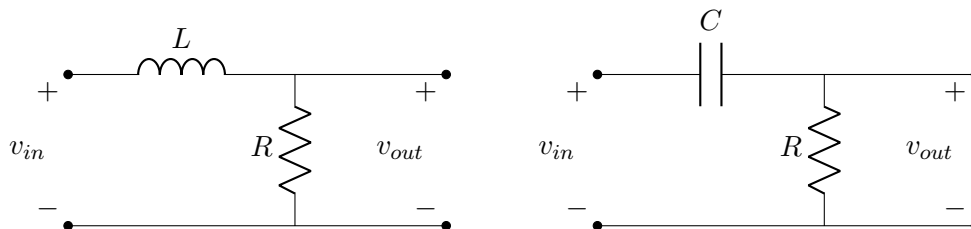**Figure 1:** Circuit diagrams for problem 2a

- The **Transfer Function** of a circuit is $H(s) = \frac{-5s}{s^2+15s+50}$. Determine the impulse response and step response of this circuit.
 - Design a circuit which produces the transfer function $H(s) = \frac{V_{out}}{V_{in}}$ equal to
 - $5(s+1)$
 - $\frac{5}{s+1}$
 - $5\frac{s+1}{s+2}$
 - $3\frac{s+50}{(s+75)^2}$
- For the following functions, sketch the Bode magnitude plots:
 - $\frac{1}{3+4s}$
 - $(1 + \frac{s}{3})(5 + s)$
 - $\frac{0.1}{(1+5s)(2+s)}$
 - $3\frac{s}{s^2+7s+10}$
 - $\frac{s^2+9s+20}{s^2(s+1)^3}$

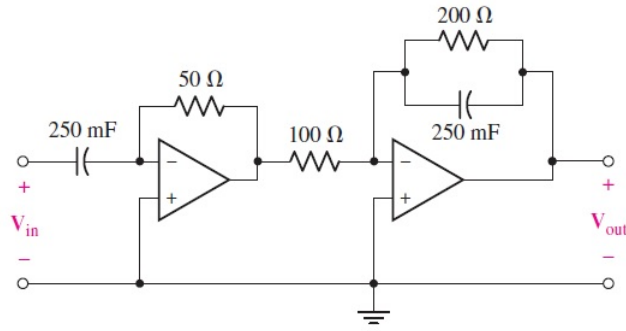4. For the circuit shown in Figure, derive an expression for the transfer function $\mathbf{H(s)} = \frac{V_{out}}{V_{in}}$. Sketch the corresponding Bode magnitude and phase plots. [20]



5. (a) Design a low-pass filter circuit with a gain of 30 dB and a cutoff frequency of 10 kHz. [5]
 (b) Design a bandpass filter having a low-frequency cutoff of 500 Hz and a high frequency cutoff of 1580 Hz. [5]
 (c) Design a low-pass filter characterized by a voltage gain of 40 dB and a corner frequency of 1000 rad/s. [5]
 (d) Design a high-pass filter characterized by a voltage gain of 25 dB and a corner frequency of 500 rad/s. [5]