

**Electrical Network Analysis (EE-241)**


Assignment # 2, Spring 2021

Submission Deadline: Wednesday April 21, 2021

Maximum Marks: 100

- Scan all the pages in the required sequence and post on the Google Classroom as a single pdf file.


1. For the circuit shown in Figure 1, determine  $i_C(0^-)$ ,  $i_L(0^-)$ ,  $i_R(0^-)$ ,  $v_C(0^-)$ ,  $i_C(0^+)$ ,  $i_L(0^+)$ ,  $i_R(0^+)$ ,  $v_C(0^+)$ , and  $v_C(t)$ . [20]

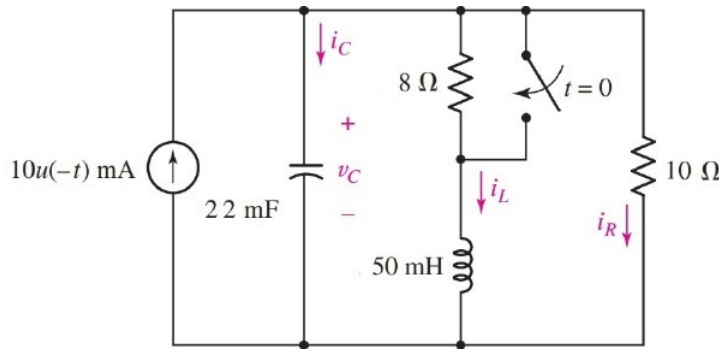

**Figure 1:** Circuit for problem 1


2. For the circuit of Figure 2,

- Obtain an expression for  $v_C(t)$  valid for all  $t > 0$ . [10]
- Determine  $v_C(t)$  at  $t = 10$  ms and  $t = 600$  ms. [4]
- Replace the  $1\ \Omega$  resistor with a  $100\text{ m}\Omega$  resistor, and the  $5\ \Omega$  resistor with a  $200\text{ m}\Omega$  resistor. Assuming the passive sign convention, obtain an expression for the capacitor current which is valid for  $t > 0$ . [6]

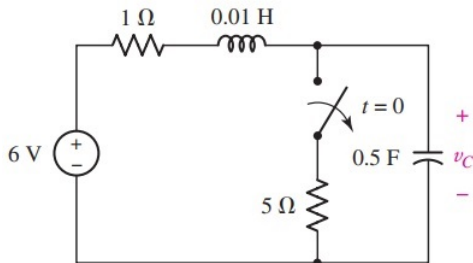


**Figure 2:** Circuit for problem 2

- Assuming there are no longer any transients present, determine the current labeled  $i_L$  of Figure 3. Express your answer as a single sinusoid. [10]
  - Calculate the power dissipated in the  $2\ \Omega$  resistor of Figure 4 assuming there are no transient present. Express the answer in terms of a single sinusoidal function. [10]

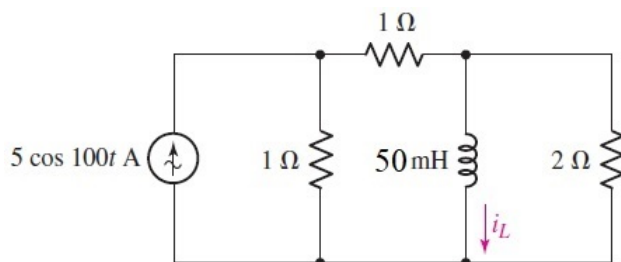


**Figure 3:** Circuit for problem 3

4. (a) Assume that  $v_s = V_m \cos \omega t$  is applied to a series RC circuit. Derive the voltage response across the capacitor. [10]
- (b) Using the equation derived in part (a) to find the steady-state expression for  $v_c(t)$  if  $v_s = 20 \sin 100t$ ,  $R = 10 \Omega$  and  $C = 100 \mu\text{F}$ . [5]
- (c) Insert an appropriate complex source into the circuit of part (b) and use it to determine the steady state expressions for  $i_C(t)$  and  $v_C(t)$ . [5]

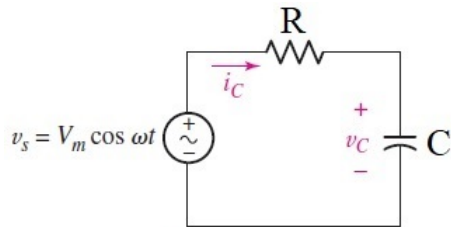


**Figure 3 :** Circuit for problem 4

5. (a) For the circuit shown in Figure 4, if  $i_s = 2 \cos 20t$  A, use a suitable complex source replacement to obtain a steady-state expression for  $i_L(t)$ . [10]

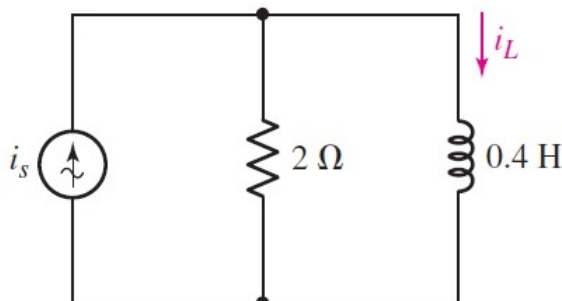

**Figure 4:** Circuit for problem 5

- (b) Employ a suitable complex source to determine the steady-state current  $i_L$  in the circuit of Figure 5. [10]

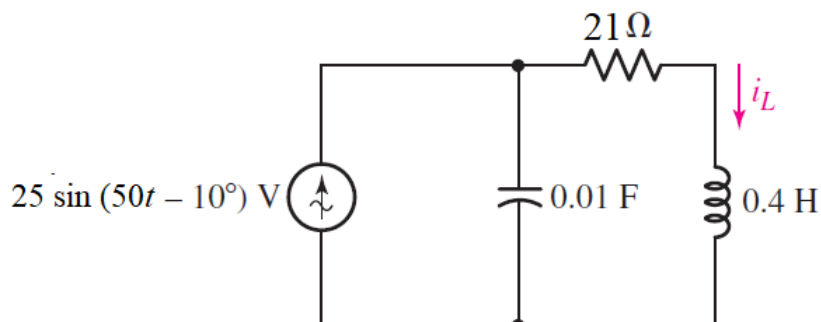

**Figure 5:** Circuit for problem 5b