

Electrical Network Analysis (EE-241)

Assignment # 3, Spring 2021

Submission Deadline: Thursday April 29, 2021 (11:59 pm) Maximum Marks: 100

- Solve all the 10 problems. (Each problem carries 10 marks).
- Use A-4 Size blank pages to solve all the problems.
- Write down your roll numbers on the first page at the top right corner.
- Scan your document carefully with the right sequence before uploading.
- **No plagiarism will be tolerated.**

1. A sinusoidal voltage is given by the expression $v(t) = 20 \cos (10t + 45^\circ)$.
 - (a) What is the time period of the voltage (in milliseconds)? [2]
 - (b) What is the frequency (in Hertz)? [2]
 - (c) What is the magnitude of voltage at $t = 10$ ms? [2]
 - (d) What is the *rms* value of v ? [2]
 - (e) Write the voltage $v(t)$ in phasor form \mathbf{V} . [2]
2. Determine the angle by which v lags the current if $v = 10 \cos (25t - 50^\circ)$.
 - (a) $i_1 = 10 \cos (25t)$ [2]
 - (b) $i_2 = 10 \cos (25t - 78^\circ)$ [2]
 - (c) $i_3 = 10 \cos (25t + 38^\circ)$ [2]
 - (d) $i_4 = 10 \sin (25t - 19^\circ)$ [2]
 - (e) $i_5 = 10 \sin (25t + 39^\circ)$ [2]
3. Find the time-domain expression corresponding to each phasor:
 - (a) $\mathbf{V} = 20.53 \angle -48^\circ \text{ V}$ [2]
 - (b) $\mathbf{I} = (10 \angle 45^\circ - 40 \angle 30^\circ)$ [4]
 - (c) $\mathbf{V} = 10 + j40 - 15 \angle 15^\circ$ [4]
4. Use the concept of phasor to combine the following sinusoidal functions into a single trigonometric expression:
 - (a) $x(t) = 90 \sin (50t - 20^\circ) + 60 \cos (50t - 70^\circ)$ [2]
 - (b) $y(t) = 10 \cos (\omega t + 30^\circ) - 10 \sin (\omega t) + 10 \cos (\omega t + 150^\circ)$ [4]
 - (c) $z(t) = 20 \sin (2000t + 40^\circ) - 10 \cos (2000t - 60^\circ)$ [4]

5. The current in a 10 mH inductor is $10 \cos(25t - 80^\circ)$ mA. Calculate
- (a) the inductive reactance. [2]
 - (b) the impedance of the inductor. [2]
 - (c) the phasor voltage \mathbf{V} . [2]
 - (d) the steady-state expression for $v(t)$. [2]
 - (e) the value of the voltage at $t = 10$ ms. [2]
6. The voltage across a 47 μ F capacitor is $30 \cos(2000t + 20^\circ)$ V. Calculate
- (a) the capacitive reactance. [2]
 - (b) the impedance of the capacitor. [2]
 - (c) the phasor current \mathbf{I} . [2]
 - (d) the steady-state expression for $i(t)$. [2]
 - (e) the value of the current at $t = 2$ ms. [2]
7. (a) Insert an appropriate complex source into the circuit represented in Figure 1 and use it to determine the steady-state expression for $i_C(t)$ and $v_C(t)$. [5]
- (b) Use the phasor method to verify the results of part (a). [5]

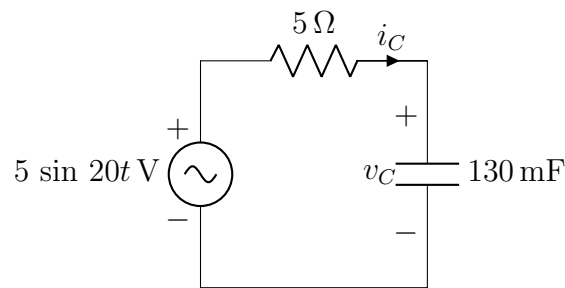


Figure 1: Circuit for problem 7

8. (a) Find the steady-state expression for v_o in the circuit of Figure 2 if $i_g(t) = 50 \cos 10000t$ mA. [5]

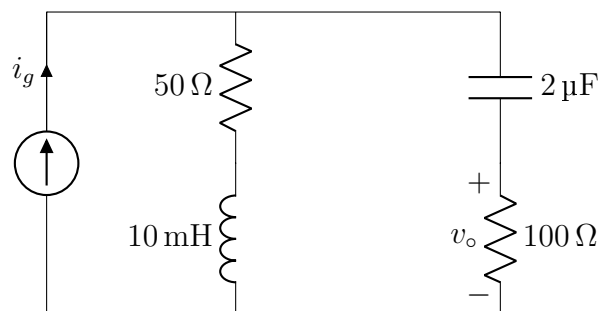


Figure 2: Circuit for problem 8a

- (b) The circuit in Figure 3 is operating in the sinusoidal steady-state. Find the value of frequency (in Hertz) if [5]

$$i(t) = 20 \sin(\omega t + 20^\circ) \text{ V},$$

$$v(t) = 20 \cos(\omega t - 16^\circ) \text{ mA}.$$

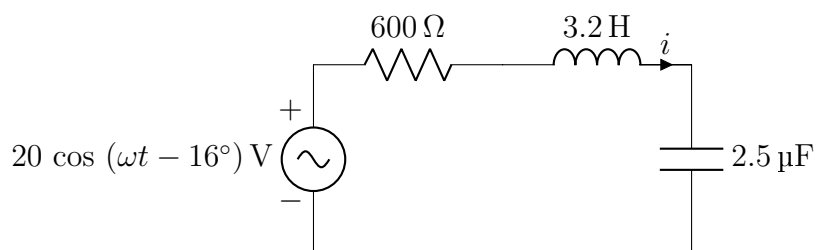


Figure 3: Circuit for problem 8b

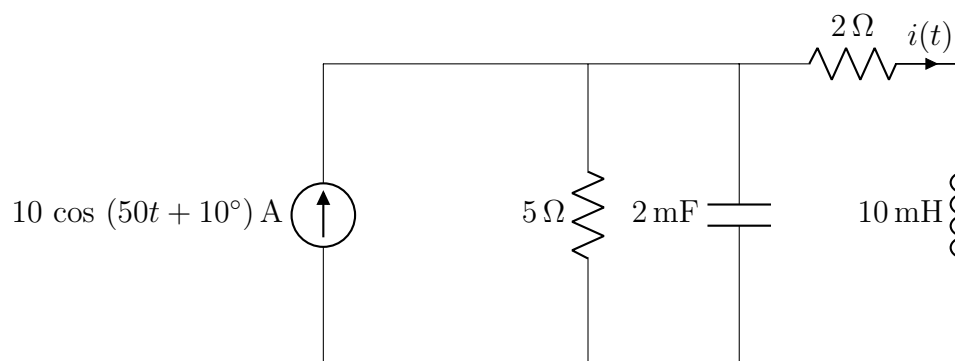


Figure 4: Circuit for problem 9a

9. (a) Use phasor-based analysis to obtain an expression for $i(t)$ in the circuit of Figure 4. [5]
 (b) The sinusoidal voltage source in the circuit in Figure 5 is $40 \sin 500t$ V. Find and draw the Thevenin equivalent with respect to terminals $a - b$. [5]

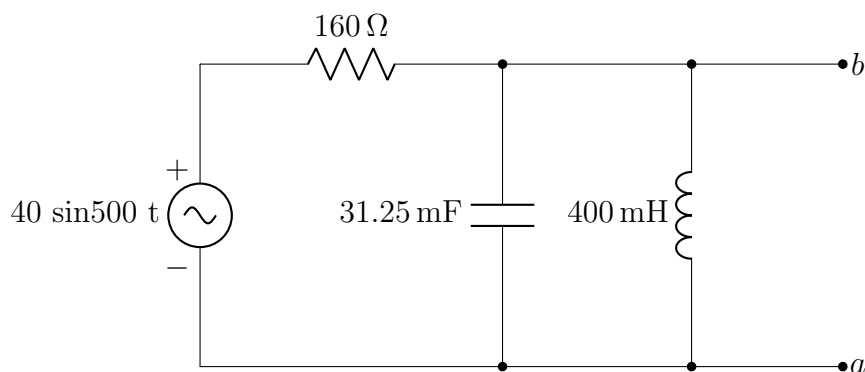


Figure 5: Circuit for problem 9b

10. For the circuit shown in Figure 6,

(a) Use nodal analysis to determine the two nodal voltages $v_1(t)$ and $v_2(t)$. [5]

(b) Use superposition theorem to verify the results of part (a). [5]

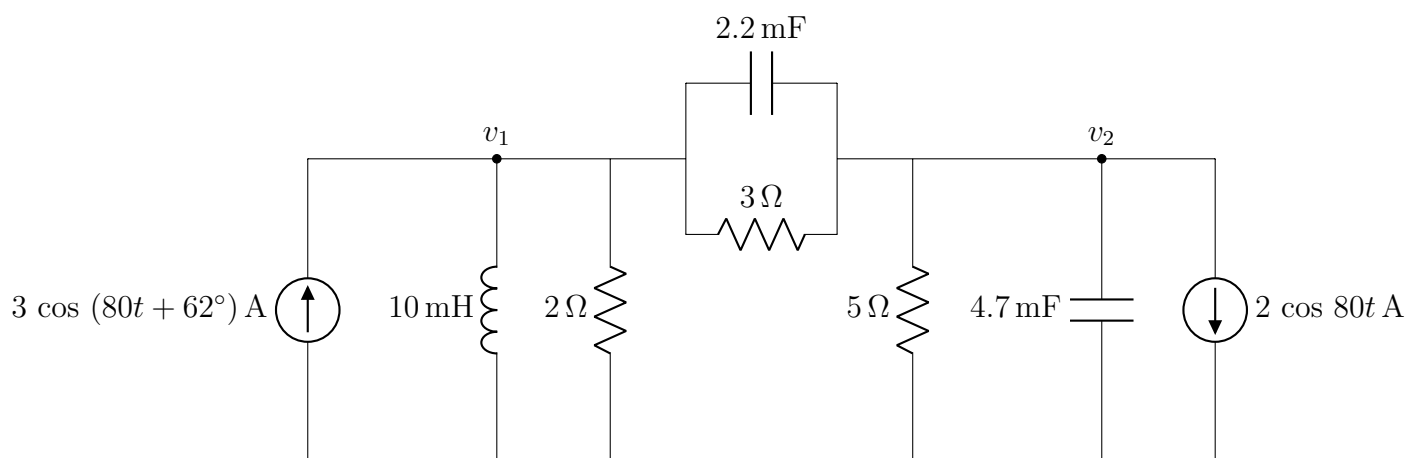


Figure 6: Circuit for problem 10