


**Electrical Network Analysis (EE-241)**

Assignment # 5, Spring 2021


Submission Deadline: **Thursday** July 01, 2021

Maximum Marks: 100

1. (a) State the complex frequency or frequencies  $s$  as well as  $s^*$  associated with each function: [4]
  - i.  $f(t) = 5e^{-10t} \cos 50t$
  - ii.  $g(t) = (4e^{-2t} - e^{-t}) \cos(5t - 93^\circ)$
  - iii.  $h(t) = 7e^{-9t} \sin(100t + 9^\circ)$
  - iv.  $i(t) = 2 \sin 60t$
- (b) Use real constants  $A, B, \theta, \phi$  etc. to construct the general form of a real time function characterized by the following frequency components: [3]
  - i.  $(10 - j3) s^{-1}$
  - ii.  $0.25 s^{-1}$
  - iii.  $0 s^{-1}, 1 s^{-1}, -j s^{-1}, (1 + j) s^{-1}$
- (c) The following voltage sources  $Ae^{Bt} \cos(Ct + \theta)$  are connected (one at a time) to a  $280 \Omega$  resistor. Calculate the resulting current at  $t = 0, 0.5$  and  $1$  s assuming passive sign convention. [4]
  - i.  $A = 1 \text{ V}, B = 0.2 \text{ Hz}, C = 0, \theta = 45^\circ$ .
  - ii.  $A = 285 \text{ mV}, B = -1 \text{ Hz}, C = 2 \text{ rad/s}, \theta = -45^\circ$ .
2. (a) For the circuit shown in Figure 4, the voltage source is chosen such that it can be represented by the complex frequency domain function  $\mathbf{V}e^{st}$ , with  $\mathbf{V} = 2.5 / -20^\circ$  and  $s = 1 + j100 s^{-1}$ . Calculate [6]
  - i.  $s^*$
  - ii. the time-domain representation of voltage  $v(t)$
  - iii. the current  $i(t)$
- (b) With regard to the circuit depicted in Figure 4, determine the time-domain voltage  $v(t)$  which corresponds to a frequency domain current of  $5 / 30^\circ \text{ A}$  for a complex frequency of  $s = (-3 + j) s^{-1}$ . [4]

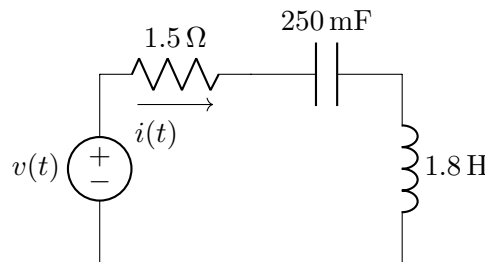
**Figure 1:** Circuit diagram for problem 2

3. (a) Find the **Laplace Transform** of  $g(t)$ ,  $h(t)$  and  $k(t)$  shown in Figure 2. [6]

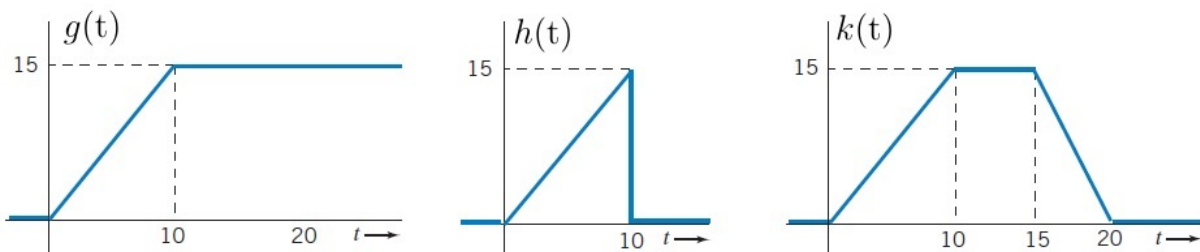**Figure 2:** Functions for problem 3a


- (b) Show that the **Laplace Transform** of the square wave is  $F(s) = \frac{1}{s(1+e^{-as})}$ . [4]

4. (a) Obtain an expression for  $\mathbf{G}(s)$  if  $g(t)$  is given by [5]
- $[5u(t)]^2 - u(t)$
  - $3e^{-2t}u(t) + 5u(t)$
  - $tu(2t)$
  - $\delta(t) + u(t) - tu(t)$
  - $2e^{-t}u(t) + 3u(t)$
- (b) Let  $i_1 = 20e^{-3t} \cos 4t$  A and  $i_2 = 30e^{-3t} \sin 4t$  A in the circuit of Figure 3. Work in the frequency domain to find  $\mathbf{V}_x$  and then find  $v_x$ . [5]

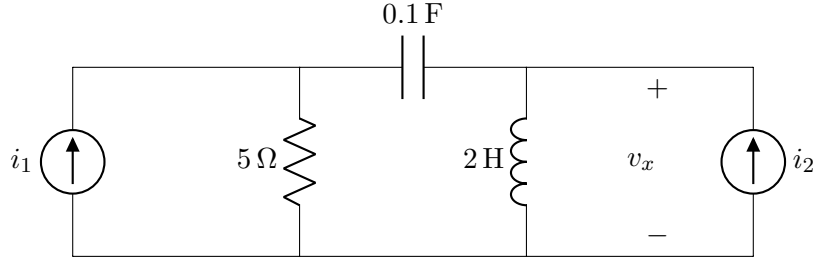


**Figure 3:** Circuit diagram for problem 4b

5. (a) Prove that  $\frac{d^2v}{dt^2} \Leftrightarrow s^2 \mathbf{V}(s) - sv(0^-) - v'(0^-)$  [2]
- (b) Prove that  $\int_{0^-}^t v(x)dx \Leftrightarrow \frac{\mathbf{V}(s)}{s}$  [2]
- (c) Prove that  $f(t-a)u(t-a) \Leftrightarrow e^{-as} \mathbf{F}(s)$  [2]
- (d) Show that  $\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} [s\mathbf{F}(s)]$  [2]
- (e) Show that  $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} [s\mathbf{F}(s)]$  [2]
6. (a) Apply the **initial or the final-value theorem** as appropriate to determine  $f(0^+)$  and  $f(\infty)$  for the following functions:
- $\frac{1}{s^2(s+4)^2(s+6)^3} - \frac{2s^2}{s} + 9$  [2]
  - $\frac{4s^2+1}{(s+1)^2(s+2)^2}$  [2]
- (b) Find the **Inverse Laplace Transform** of the functions  $\frac{s+3}{s^2+7s+10}$  and  $\frac{10}{(s^2+6s+10)(s+2)}$  [3+3]
7. (a) Assuming zero initial conditions in Figure 4, find  $i(t)$  and  $v(t)$ .
- In time-domain. [3]
  - Working initially in the s-domain and then converting back to time domain. [3]

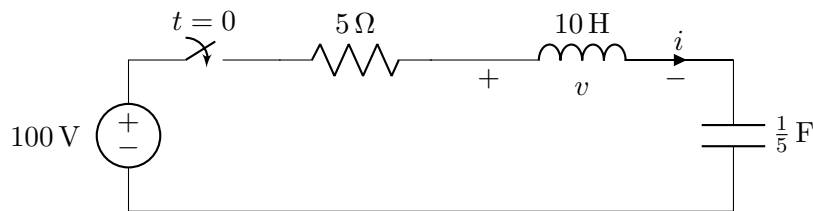


**Figure 4:** Circuit diagram for problem 7a

- (b) In the circuit of Figure 5,  $v(0^-) = 1.2$  V and  $i(0^-) = 0.4$  A. Find  $v(t)$  and  $i(t)$  for  $t > 0$ . [4]

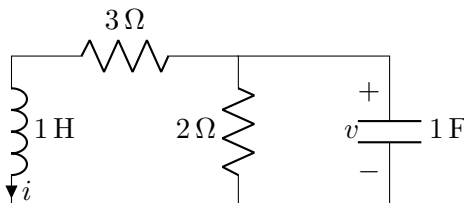


**Figure 5:** Circuit diagram for problem 7b

8. (a) Using either **Thevenin's** or **Norton's Theorem**, determine an equivalent network for the terminals  $a - b$  in the Figure 6 for zero initial conditions. What will be the current in a  $1\text{ F}$  capacitor if connected between terminals  $a - b$ ? [2]

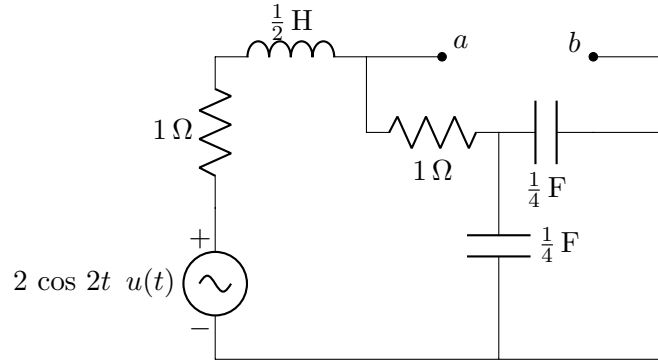


**Figure 6:** Circuit diagram for problem 8a

- (b) For the circuit of Figure 7, the switch  $S$  is closed at  $t = 0$ , a steady state having previously existed. Find the expression for the current in the resistor  $R$  for  $t > 0$ . You may use any Network Theorem. [4]

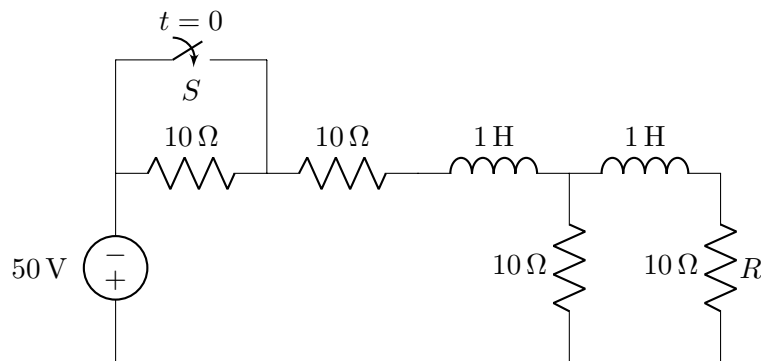

**Figure 7:** Circuit diagram for problem 8b


- (c) For the circuit shown in Figure 8, obtain an expression for  $v_x(t)$ . [4]

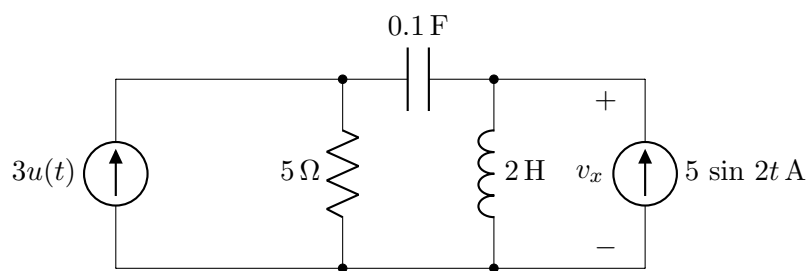

**Figure 8:** Circuit diagram for problem 8c

9. (a) Let  $h(t) = 2e^{-3t}u(t)$  and  $x(t) = u(t) - \delta(t)$ . Find  $y(t) = h(t) \star x(t)$  by [2]
- using convolution in the time domain
  - finding  $H(s)$  and  $X(s)$  and then obtaining inverse Laplace Transform of  $H(s)X(s)$
- (b) If a network is found to have the transfer function  $H(s) = \frac{s}{s^2 + 8s + 7}$ , determine the s-domain output voltage for  $v_{in}(t)$  equal to [4]
- $3u(t)\text{ V}$
  - $25e^{-2t}u(t)\text{ V}$
  - $4u(t + 1)\text{ V}$
  - $2 \sin 5t\text{ V}$

- (c) A particular network is known to be characterized by the transfer function  $H(s) = \frac{s+1}{s^2+23s+60}$ . Determine the critical frequencies of the output if the input is
- $2u(t) + 4\delta(t)$
  - $-5e^{-t}u(t)$
  - $4te^{-2t}u(t)$
  - $5\sqrt{2}e^{-10t}\cos 5t u(t)$
10. (a) For each of the two networks shown in Figure 9, write the **Transfer Functions**  $H(s)$  and determine their **poles** and **zeros**. [2]

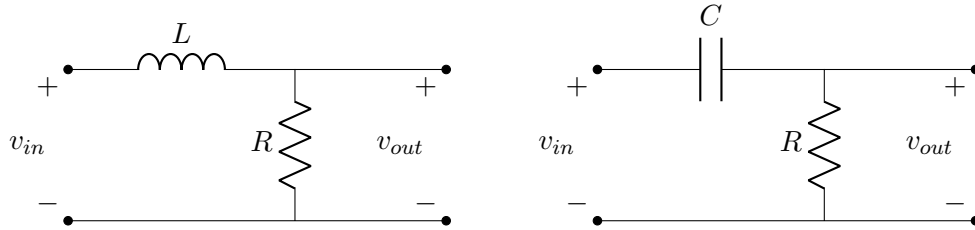

**Figure 9:** Circuit diagrams for problem 10a

- (b) The **Transfer Function** of a circuit is  $H(s) = \frac{-5s}{s^2+15s+50}$ . Determine the impulse response and step response of this circuit. [4]
- (c) Design a circuit which produces the transfer function  $H(s) = \frac{V_{out}}{V_{in}}$  equal to [4]
- $5(s+1)$
  - $\frac{5}{s+1}$
  - $5\frac{s+1}{s+2}$
  - $3\frac{s+50}{(s+75)^2}$